
 Marwadi University	Marwadi University Faculty of engineering and technology Department of Information and Communication Technology	
Subject: VLSI Design	AIM: Design and Implementation of Digital Circuits in Microwind	
LONG HOUR DESIGN	Date: 13/09/2025	Enrollment No:92410133045

1. 4-Bit Full Adder

A 4-bit Full Adder is designed to generate a 4-bit Sum and is designed by combining four 2-bit Full Adders and the Four bits output along with the Carry Bit.

Circuit Diagrams: -

Truth Tables: -

 

Input			Output	
A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Logic Equations: -

The sum (S) of the full-adder is the XOR of A, B, and Cin. Therefore,



$$\text{Sum, } S = A \oplus B \oplus C_{in} = A'B'C_{in} + A'BC'_{in} + AB'C'_{in} + ABC_{in}$$


The carry (C) of the half-adder is the AND of A and B. Therefore,

$$\text{Carry, } C = AB + AC_{in} + BC_{in}$$

 Marwadi University	Marwadi University Faculty of engineering and technology Department of Information and Communication Technology	
Subject: VLSI Design	AIM: Design and Implementation of Digital Circuits in Microwind	
LONG HOUR DESIGN	Date: 13/09/2025	Enrollment No:92410133045

Screenshots Of Layouts: -

  


 Marwadi University	Marwadi University Faculty of engineering and technology Department of Information and Communication Technology	
Subject: VLSI Design	AIM: Design and Implementation of Digital Circuits in Microwind	
LONG HOUR DESIGN	Date: 13/09/2025	Enrollment No:92410133045

2. 8×1 Multiplexer

The 8×1 Multiplexer is made using 4×1 Multiplexers and 2×1 Multiplexer. We know that 4×1 Multiplexer has 4 data inputs, 2 selection lines and one output. Whereas, 8×1 Multiplexer has 8 data inputs, 3 selection lines and one output.

Circuit Diagrams: -

 

Block Diagram: -

 



Figure 4 - 8:1 Multiplexer

Truth Tables: -



Selection Inputs			Output
S ₂	S ₁	S ₀	Y
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆
1	1	1	I ₇


 Marwadi University	Marwadi University Faculty of engineering and technology Department of Information and Communication Technology	
Subject: VLSI Design	AIM: Design and Implementation of Digital Circuits in Microwind	
LONG HOUR DESIGN	Date: 13/09/2025	Enrollment No:92410133045

Logic Equations: -

$$Y = S_2S_1S_0I_0 + S_2S_1S_0I_1 + S_2S_1S_0I_2 + S_2S_1S_0I_3 + S_2S_1S_0I_4 + S_2S_1S_0I_5 + S_2S_1S_0I_6 + S_2S_1S_0I_7$$

Screenshots Of Layouts: -

  


 Marwadi University	Marwadi University	
	Faculty of engineering and technology	
	Department of Information and Communication Technology	
Subject: VLSI Design	AIM: Design and Implementation of Digital Circuits in Microwind	
LONG HOUR DESIGN	Date: 13/09/2025	Enrollment No:92410133045

3. 1-bit Magnitude Comparator

A 1-bit magnitude comparator circuit diagram compares two 1-bit binary inputs (A and B) and produces outputs indicating whether A is greater than, equal to, or less than B. The circuit typically uses logic gates like XOR, AND, and NOT gates to implement these comparisons. The output signals would represent the comparison outcomes: $A > B$, $A = B$, or $A < B$.

Circuit Diagrams: -

Truth Tables: -

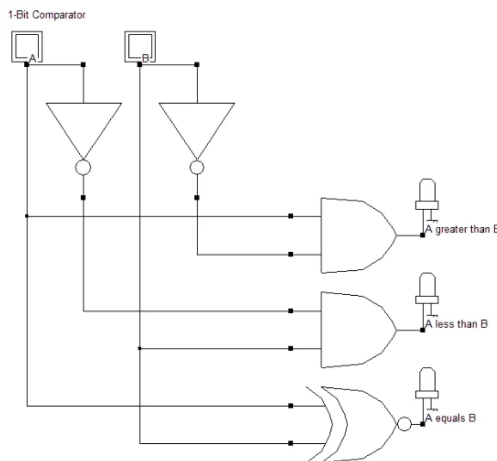

The logic circuit of a 1-bit comparator

Inputs		Outputs		
B	A	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

Logic Equations: -

$$Z = A'B' + AB$$

This is similar to the equation of an EXNOR gate. Hence,

$$Z = A \oplus B$$



Marwadi
University

Marwadi University

Faculty of engineering and technology

Department of Information and Communication Technology

Subject: VLSI Design



AIM: Design and Implementation of Digital Circuits in Microwind


LONG HOUR DESIGN

Date: 13/09/2025

Enrollment No:92410133045

Screenshots Of Layouts: -

 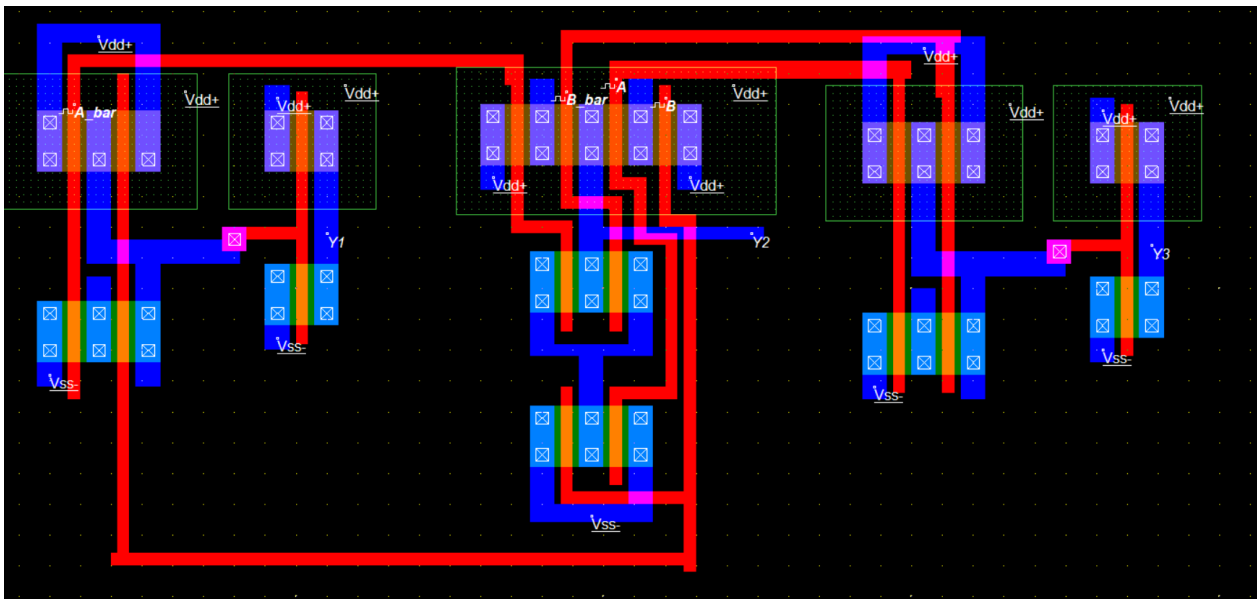


 Marwadi University	Marwadi University Faculty of engineering and technology Department of Information and Communication Technology	
Subject: VLSI Design	AIM: Design and Implementation of Digital Circuits in Microwind	
LONG HOUR DESIGN	Date: 13/09/2025	Enrollment No:92410133045

4. 4-bit Serial-In Serial-Out (SISO) Register

The term “SISO” stands for “Serial-In Serial-Out”. The SISO shift register circuit accepts serial data on its input pin and shifts it out serially on its output pin. The number of bits that can be shifted out before the next bit arrives depends on the speed of the clock signal that controls the operation of the shift register. This type of shift register can be used as a buffer between two asynchronous devices that communicate with each other using signals with different frequencies or phases.

Circuit Diagrams: -

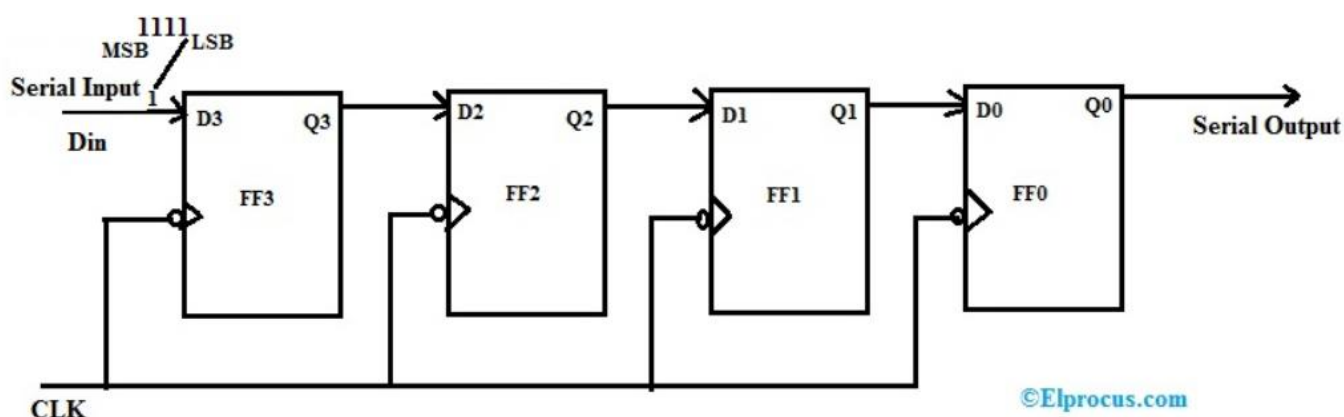

Truth Table:

Operation of the Shift-right Register					
Timing pulse	Q_A	Q_B	Q_C	Q_D	Serial output at Q_D
Initial value	0	0	0	0	0
After 1 st clock pulse	1	0	0	0	0
After 2 nd clock pulse	1	1	0	0	0
After 3 rd clock pulse	0	1	1	0	0
After 4 th clock pulse	1	0	1	1	1



Marwadi
University

Marwadi University

Faculty of engineering and technology

Department of Information and Communication Technology

Subject: VLSI Design


AIM: Design and Implementation of Digital Circuits in Microwind

LONG HOUR DESIGN


Date: 13/09/2025


Enrollment No:92410133045


Timing Diagram:

 

Screenshots Of Layouts: -

 

 Marwadi University	Marwadi University Faculty of engineering and technology Department of Information and Communication Technology	
Subject: VLSI Design	AIM: Design and Implementation of Digital Circuits in Microwind	
LONG HOUR DESIGN	Date: 13/09/2025	Enrollment No:92410133045

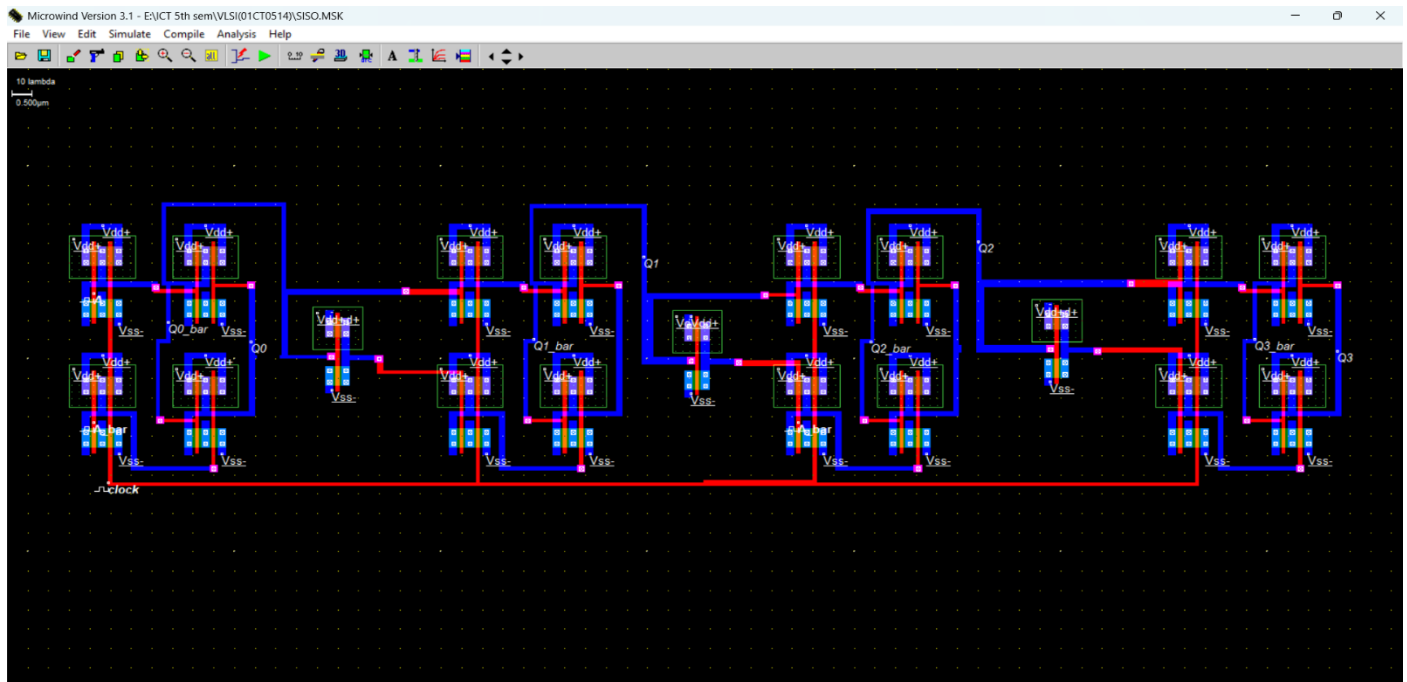

Conclusion

- Successfully designed and simulated four circuits in Microwind
- Learned transistor-level layout design and timing verification
- Future work: extend to larger adders, PIPO registers, multipliers